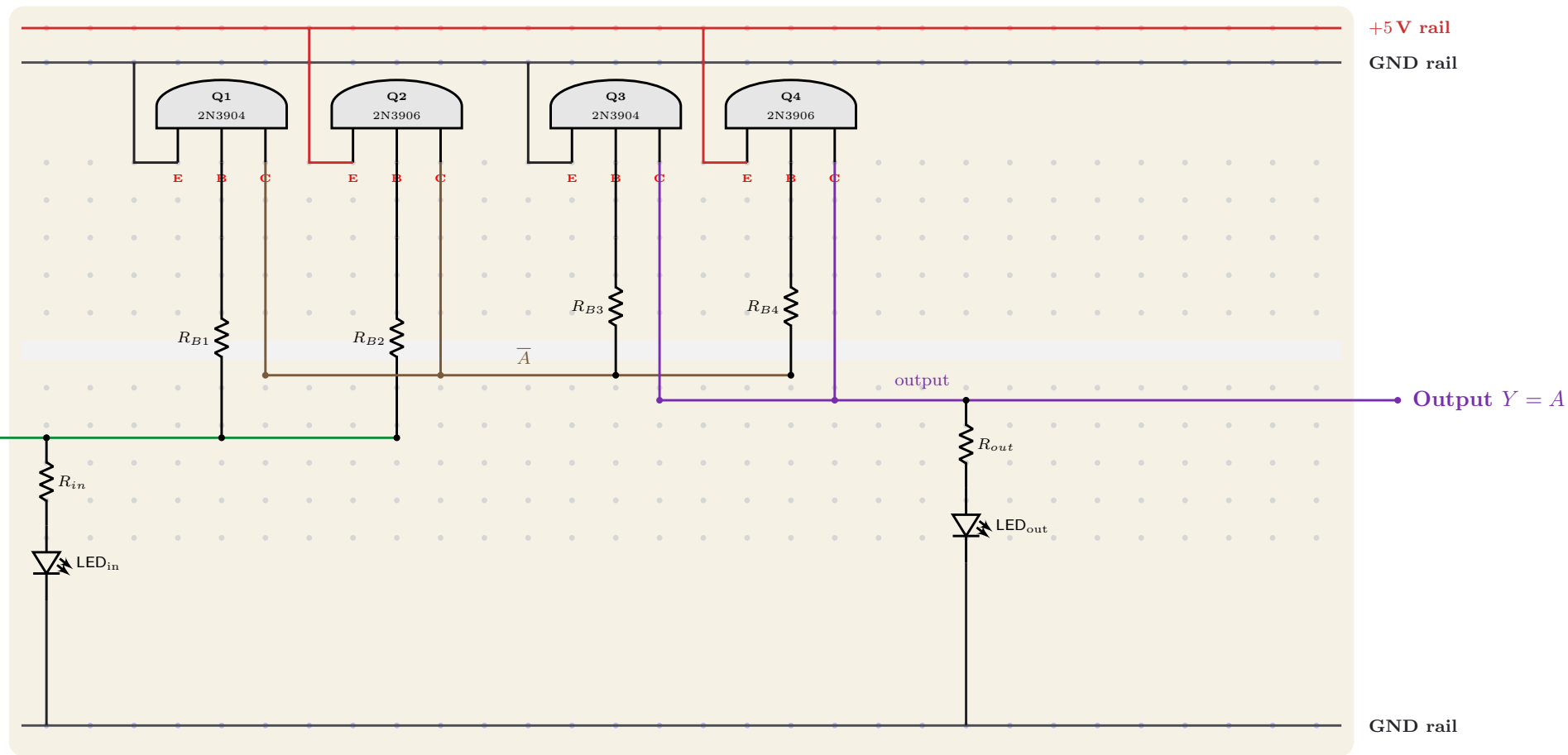




Jumper wires: — +5 V — GND — input A — $\bar{A}$ (internal) — output Y

Each column of five holes in a bank is one node; transistor legs are E B C in *adjacent* holes.

The two GND rails are *one node* – bridge them with a jumper at the board edge.